



UNIVERSITEIT•STELLENBOSCH•UNIVERSITY
jou kennisvennoot • your knowledge partner

E344 Assignment 1

Elijah Seth Cishugi

21745102

Report submitted in partial fulfilment of the requirements of the module
Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical
and Electronic Engineering at Stellenbosch University.

August 16, 2020



UNIVERSITEIT • STELLENBOSCH • UNIVERSITY
jou kennisvennoot • your knowledge partner

Plagiaatverklaring / *Plagiarism Declaration*

1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.

Plagiarism is the use of ideas, material and other intellectual property of another's work and to present it as my own.

2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.

I agree that plagiarism is a punishable offence because it constitutes theft.

3. Ek verstaan ook dat direkte vertalings plagiaat is.


I also understand that direct translations are plagiarism.

4. Dienooreenkomstig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelike aanhaal van teks sonder aanhalingstekens (selfs al word die bron volledig erken) plagiaat is.

Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism

5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.

21745102	
Studentenommer / <i>Student number</i>	Handtekening / <i>Signature</i>
E.S Cishugi	August 16, 2020
Voorletters en van / <i>Initials and surname</i>	Datum / <i>Date</i>

Contents

Declaration	i
List of Figures	iii
List of Tables	iv
Nomenclature	v
1. System design	1
1.1. System overview	1
1.2. Rationale	1
2. Voltage regulation	2
2.1. Introduction	2
2.2. Design	2
2.3. Results	3
2.4. Summary	5
3. Temperature sensor conditioning circuit	6
3.1. Intro	6
3.2. Design	6
3.2.1. Low Pass Filter design	6
3.2.2. Differential Amplifier design	7
3.3. Results	8
3.4. Summary	9
4. System and conclusion	10
4.1. System	10
4.2. Lessons learnt	10
Bibliography	11
A. Social contract	12
B. GitHub Activity Heatmap	13
C. Stuff you want to include	14

List of Figures

1.1. System diagram	1
2.1. Linear regulator circuit diagram	2
2.2. Switchmode regulator circuit diagram	3
2.3. Voltage regulation simulation results	4
3.1. Low Pass Filter circuit diagram	6
3.2. Differential Amplifier circuit diagram	7
3.3. Low-pass filter frequency response	8
3.4. Low-pass filter noise suppression simulation results	8
3.5. Low-pass filter rise time simulation results	8
3.6. Full Op amp input and output range simulation results	9
3.7. Total average current of temperature sensor circuit simulation results	9

List of Tables

2.1. Efficiency and power calculation	4
3.1. measured full Op Amp input and output ranges	9
4.1. Temperatures and corresponding output voltage	10

Nomenclature

Variables and functions

$p(x)$	Probability density function with respect to variable x .
$P(A)$	Probability of event A occurring.
ε	The Bayes error.
ε_u	The Bhattacharyya bound.
B	The Bhattacharyya distance.
s	An HMM state. A subscript is used to refer to a particular state, e.g. s_i refers to the i^{th} state of an HMM.
\mathbf{S}	A set of HMM states.
\mathbf{F}	A set of frames.
\mathbf{o}_f	Observation (feature) vector associated with frame f .
$\gamma_s(\mathbf{o}_f)$	A posteriori probability of the observation vector \mathbf{o}_f being generated by HMM state s .
μ	Statistical mean vector.
Σ	Statistical covariance matrix.
$L(\mathbf{S})$	Log likelihood of the set of HMM states \mathbf{S} generating the training set observation vectors assigned to the states in that set.
$\mathcal{N}(\mathbf{x} \mu, \Sigma)$	Multivariate Gaussian PDF with mean μ and covariance matrix Σ .
a_{ij}	The probability of a transition from HMM state s_i to state s_j .
N	Total number of frames or number of tokens, depending on the context.
D	Number of deletion errors.
I	Number of insertion errors.
S	Number of substitution errors.

Acronyms and abbreviations

AE	Afrikaans English
AID	accent identification
ASR	automatic speech recognition
AST	African Speech Technology
CE	Cape Flats English
DCD	dialect-context-dependent
DNN	deep neural network
G2P	grapheme-to-phoneme
GMM	Gaussian mixture model
HMM	hidden Markov model
HTK	Hidden Markov Model Toolkit
IE	Indian South African English
IPA	International Phonetic Alphabet
LM	language model
LMS	language model scaling factor
MFCC	Mel-frequency cepstral coefficient
MLLR	maximum likelihood linear regression
OOV	out-of-vocabulary
PD	pronunciation dictionary
PDF	probability density function
SAE	South African English
SAMPA	Speech Assessment Methods Phonetic Alphabet

Chapter 1

System design

1.1. System overview

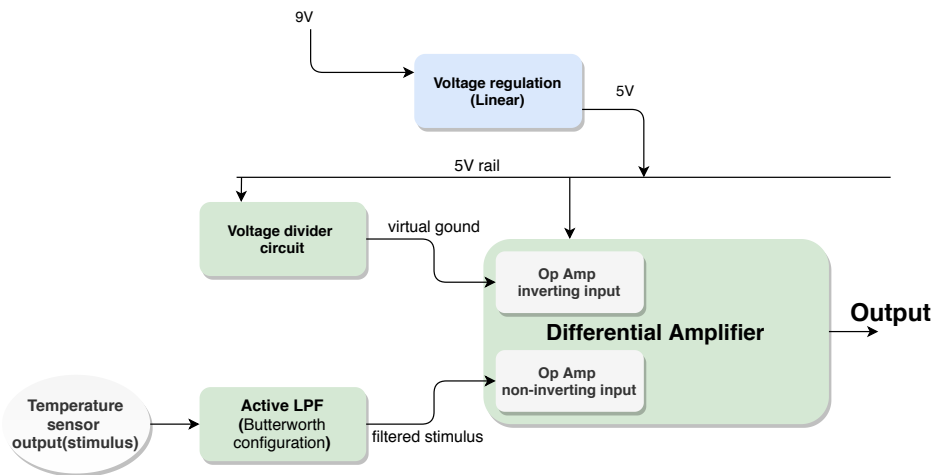


Figure 1.1: System diagram

The purpose of this design is to implement a signal conditioning circuit for an analogue temperature sensor. The **voltage regulator** shall provide a regulated 5V supply to the circuit from a nominal 9V power. An Op Amp circuit in a **differential amplifier** configuration is used: It provides a gain and removes a dc offset from the sensor output(stimulus) and thus, amplifies it from millivolts to volts while staying in the recommended output voltage range. In order to remove the dc offset from the stimulus and establish a virtual ground, given that only a positive voltage rail shall be used to power the Op Amp, a **voltage divider**(a resistors circuit) is used. Before feeding the stimulus to the amplifier, an **active low-pass filter** in the Butterworth configuration is used. The filter shall suppress noise from the stimulus by attenuating components at 50Hz and above.

1.2. Rationale

A linear regulator was chosen over a switching mode regulator due to the low noise levels on its output despite the switching regulator being more power efficient than the linear one. A second order Butterworth low-pass filter has high accuracy, low noise levels, relatively short settling time and a sharp drop-off gradient after the cut-off frequency(approximately 40db/dec): these characteristics make it an ideal choice for a filter given that noise need to be suppressed from the stimulus at 50Hz without attenuating the dc components.

Chapter 2

Voltage regulation

2.1. Introduction

This section deals with the power conditioning of the circuit. Two alternatives were available; namely a linear voltage regulator, the LM7805 or a switching mode regulator, the LM2595. The linear regulator's resistance varies according to the load and results in a constant output voltage. Conversely, switching regulators rapidly switch a series element(FETs) on and off. These devices store the input energy temporarily and then release that energy to the output at a different voltage level. [1]

The following subsection documents the rationale followed in the choice of the regulator.

2.2. Design

In order to pick which one of the regulators in the design, both the linear and switching mode regulators were implemented with additional circuitry and their respective performances were compared.

- **Linear regulation**

The circuit diagram is illustrated in figure 2.1 bellow. Capacitors C1 and C2 are used to smooth out noise on the 9V input supply and the 5V regulated output, respectively.

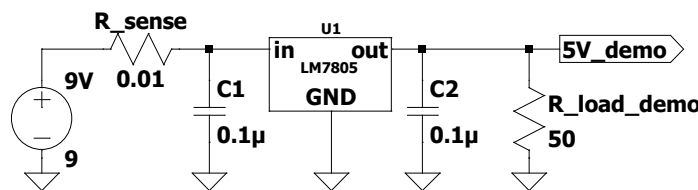


Figure 2.1: Linear regulator circuit diagram

Capacitors C1 and C2 values, 0.1 μ F each, were selected as suggested in the LM7805 data sheet specifications for typical applications circuits for a minimal noise linear regulation. [2]

- **Switch mode regulation**

The circuit diagram as derived from the LM2595 data sheet [3]. is illustrated in figure 2.2 bellow.

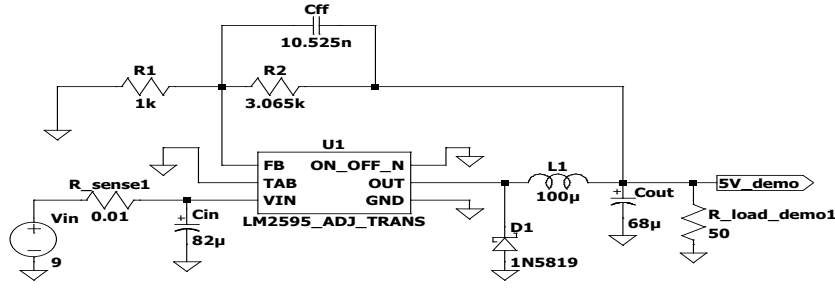


Figure 2.2: Switchmode regulator circuit diagram

The configuration is for an adjustable output voltage and it was preferred to a fixed output voltage for more flexibility.

In both the linear and switching regulator evaluations, a resistive load, R_{load_demo} was used to draw 100mA from the 5VDC side. Hence, $R_{load_demo} = \frac{5V}{100mA} = 50\Omega$

- R_1 and R_2 :

$$R_1 = 1k\Omega, R_2 = R_1 \left(\frac{V_{OUT}}{V_{REF}} - 1 \right), \text{ where } V_{REF} = 1.23V.$$

$$\therefore R_2 = 3,065k\Omega$$

These 2 resistors set the output voltage value to the required 5V.

- Catch Diode D1: A Schottky diode, the 1N5819 was picked due to its fast switching speed and low forward voltage drop.

- Capacitors C_{in} and C_{out} values were selected following the quick design table for a 5VDC output [3].


- FeedFoward Capacitor C_{ff} : Although this capacitor is only required for an output voltage greater than 10V, adding it substantially reduces noise levels at the regulator output, hence it was retained in the design. $C_{ff} = \frac{1}{31 \times 10^3 \times R_2}$

$$\therefore C_{ff} = 10.5nF$$


- L1: from the given formula $E \cdot T = (V_{IN} - V_{OUT} - V_{SAT}) \cdot \frac{V_{OUT} + V_D}{V_{IN} - V_{SAT} + V_D} \cdot \frac{1000}{150kHz} (V \cdot \mu s)$, where $V_{SAT} = 1V$ and table 30 in the data sheet [3], L1 value was chosen to be 100 μF . With the linear and switchmode regulators designed as above, a 5VDC regulated output was expected through simulations. The following subsection documents the obtained results.

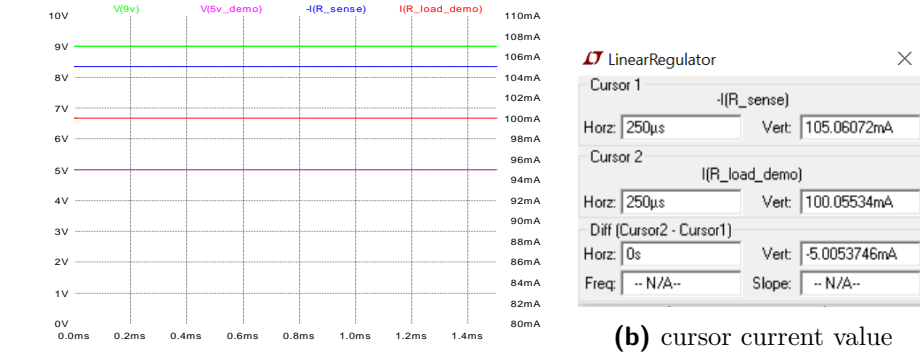2.3. Results


To select the adequate regulator(linear or switchmode), simulations were performed on the above two designs in order to asses their conformity to the expected results as well as the output noise levels and efficiencies of the regulators. Figure 2.3 bellow illustrates the simulation results:



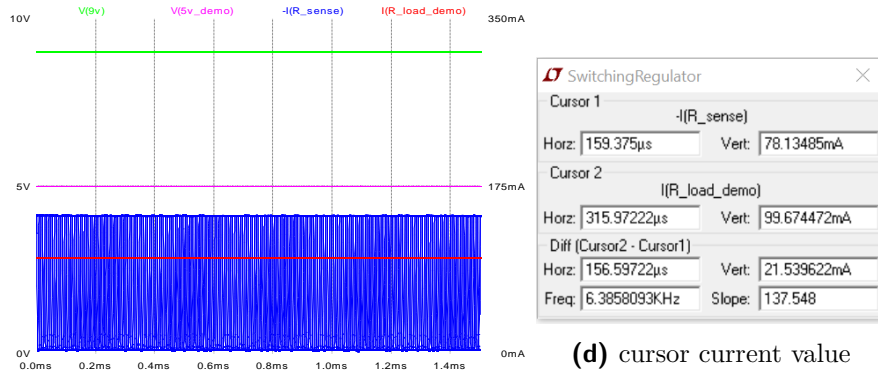(a) Linear regulator input and output voltages and currents



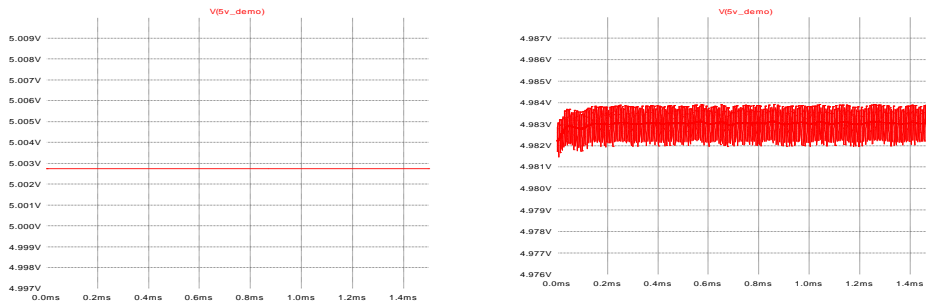(c) Switchmode regulator input and output voltages and currents



(e) Linear regulator output noise level (f) Switchmode regulator output noise level

Figure 2.3: Voltage regulation, comparing the linear and Switchmode regulators

In addition, the difference between the input and output currents vary between the two regulator, which causes their power efficiency to differ. Efficiency and power calculation is illustrated in 2.1 bellow.

Regulator	Input Voltage	Input Current	Input Power	Output Voltage	Output Current	Output Power	Efficiency	Dropout Voltage
Linear	9VDC	105.06mA	945.547mW	5.003VDC	100mA	500.3mW	52.91%	2V
Switchmode	9VDC	60.23mA(rms)	560.03mW	5.00VDC	100.01mA	501.5mW	89.55%	0.1V

Table 2.1: Efficiency and power calculation

2.4. Summary

As expected, both the liner and switching mode regulators output 5VDC with 100 mA into the $50\ \Omega$ demo load. However, the switching mechanism in the switchmode regulator introduces lots of noise (approximately 1.61 mVpp) on its output despite the regulator's high efficiency (89.55%) and very low dropout voltage (0.1 V). Inversely, the linear regulator has very low output noise levels (practically none) but with low efficiency (52.91 %) and relatively high dropout voltage (2 V), meaning the input voltage needs to be at least 7 V for the regulation to occur. Given its low output noise levels, the liner regulator was preferred to the switchmode one. In addition, despite the linear regulator low efficiency, the power loss is approximately 445.25 mW for the 100 mA output current. A thermal analysis in the above condition resulted in junction temperature of 53.94 degrees which is way smaller than the the 125 degree maximum rated. Keeping in mind that the circuit will operate at less than 50 mA output current, we can thus expect less power loss in the linear regulator.

Chapter 3

Temperature sensor conditioning circuit

3.1. Intro

This section documents the design of the of the temperature sensor conditioning circuitry. It includes a differential amplifier and an active low pass filter.

3.2. Design

3.2.1. Low Pass Filter design

An active low pass filter in the Butterworth configuration was selected. It has a fast step response as well a steep amplitude drop-of gradient after the corner (3dB) frequency. The circuit digram is illustrated in figure 3.1 bellow.

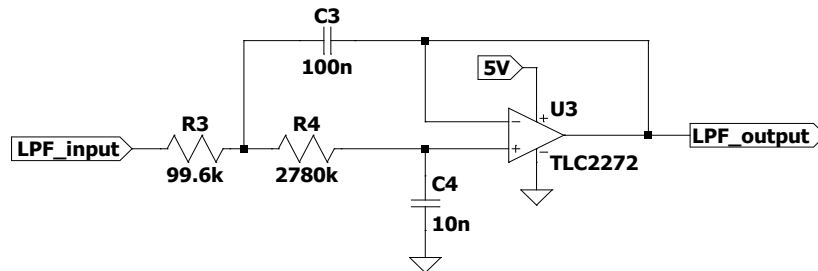


Figure 3.1: Low Pass Filter circuit diagram

Designing the above circuit involved selecting values for capacitors C3 and C4 and resistors R3 and R4 for a corner frequency of 5Hz. Given that it's a second order low pass filter we can thus expect the signal at 50Hz (10 times the corner frequency) to be attenuated by -30 to -40dB. With a -30dB attenuation, the 15mV amplitude (corresponding to 1 degree C as per specifications) noise signal will be attenuated to 0.5mV amplitude. Given that the differential amplifier has a gain of 41, this will ensure that the gain at the final output is at most $41 \times 0.5\text{mV} = 20.5\text{mVp}$ which is smaller than the required 80 mVp.

- Select $C4 = 10\text{ nF}$; then choose $C3 = 10 \times C4 = 100\text{ nF}$ for a faster step response.
- Select $R4 = 2780\text{ k}\Omega$; With $C4$, $C3$ and $R4$ fixed, the only degree of freedom left is on $R3$, which is computed below for a 5Hz cut-off frequency:

$$f_c = \frac{1}{2\pi \cdot \sqrt{C3 R3 C4 R4}}$$

$$R4 = \frac{1}{f_c^2 \cdot (2\pi)^2 C3 R3 C4} = \frac{1}{5^2 (2\pi)^2 \cdot 100 \cdot 10^{-9} \cdot 10 \cdot 10^{-9} \cdot 2780 \cdot 10^3}$$

$\therefore R4 = 99,6\text{ k}\Omega$, resulting Bandwidth: 5Hz and rise time of approximately 83.91 ms.

3.2.2. Differential Amplifier design

A non inverting differential amplifier configuration was used. The circuit features a reference voltage or virtual ground, used given that only a positive supply was used to power the amplifier. Having a virtual ground allows to remove the DC offset from the sensor output(stimulus) corresponding to temperatures bellow 34°C and introduce a DC offset in the amplifier output, thus allowing the use of the full 0 to 5V swing. The circuit diagram is illustrated in figure 3.2 bellow:

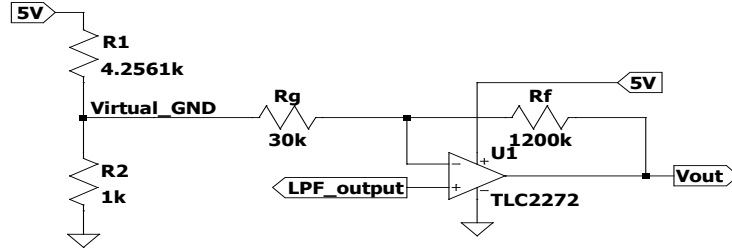


Figure 3.2: Differential Amplifier circuit diagram

- R_f and R_g : for amplifier gain

Input swing 930mV(34°C) to 1050mV(42°C) or 120mV swing. Targeted output swing: 0.1 to 4.9V or 4.8Vpp. Hence gain $\alpha = \frac{4.8V}{120mV} = 40 = \frac{R_f}{R_g}$

Select $R_f = 1200k\Omega$ (large enough to limit current consumption), hence, $R_g = \frac{1200k\Omega}{40}$

$$\therefore R_g = 30k\Omega$$

- R_1 and R_2 : for virtual ground design

V^+ and V^- symbols used bellow correspond to the inverting and non-inverting inputs of the op Amp respectively.

$$\text{KCL at } V^-: \frac{V^- - V_{\text{virtual_GND}}}{R_g} + \frac{V^- - V_{\text{out}}}{R_f} = 0$$

$$\therefore V_{\text{out}} = \left(\frac{R_f}{R_g} + 1 \right) V^- - \frac{R_f}{R_g} \cdot V_{\text{virtual_GND}}$$

$$V^- = V^+ = V_{\text{LPF_out}} \text{ (Ideal Op Amp)}$$

$$\therefore V_{\text{out}} = \left(\frac{R_f}{R_g} + 1 \right) V_{\text{LPF_out}} - \frac{R_f}{R_g} \cdot V_{\text{virtual_GND}}$$

The goal is to remove the DC component from the amplifier input $V_{\text{LPF_out}}$, 990mV corresponding to 38°C and introduce a 2.5VDC offset at the output for an optimal swing.

$$\therefore \left(\frac{R_f}{R_g} + 1 \right) \cdot V_{\text{DC}} - \frac{R_f}{R_g} \cdot V_{\text{virtual_GND}} = 2,5$$

$$\therefore \left(\frac{1200}{30} + 1 \right) \cdot 0,990 - \frac{1200}{30} \cdot V_{\text{virtual_GND}} = 2,5$$

$$\therefore V_{\text{virtual_GND}} = 0.9525 \text{ V}$$

Select $R_1 = 1kV$

$$V_{\text{virtual_GND}} = \frac{R_1}{R_1 + R_2} \cdot 5$$

$$\therefore 0,95225 = \frac{1000}{1000 + R_2} \cdot 5$$

$$\therefore R_2 = 4,2561k\Omega$$

In addition, with $V_{\text{virtual_GND}} = 0.9525 \text{ V}$, the voltage at V^- will at most be 0.9525 V($V_{\text{IN_max}}$) and 930mV(corresponding to 34°C and noise)($V_{\text{IN_min}}$)is the manimum input at V^+ ; This falls well within the TLC2272 common-mode input voltage range of -0.3 to 4V [4].

3.3. Results

Figures 3.3, 3.4, 3.5, 3.6 and 3.7 bellow documents the simulation results for both the Low-pass filter and the differential amplifier.

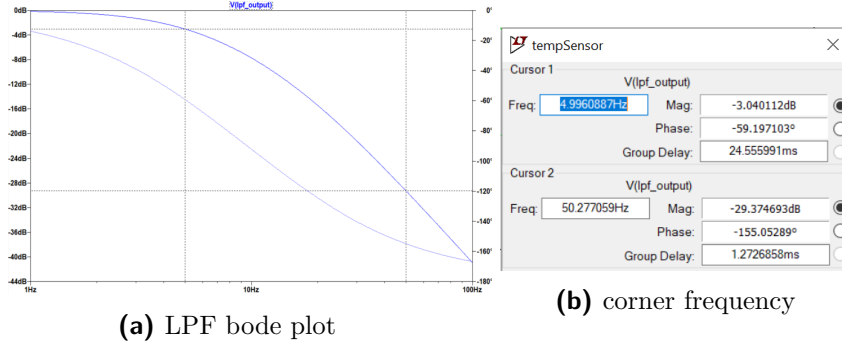


Figure 3.3: Bode plot: corner frequency and amplitude response at 50Hz

As designed for, the bandwidth(corresponding to the corner frequency) is 5Hz and the attenuation at 50Hz is -29.37dB(close to the expected -30dB).

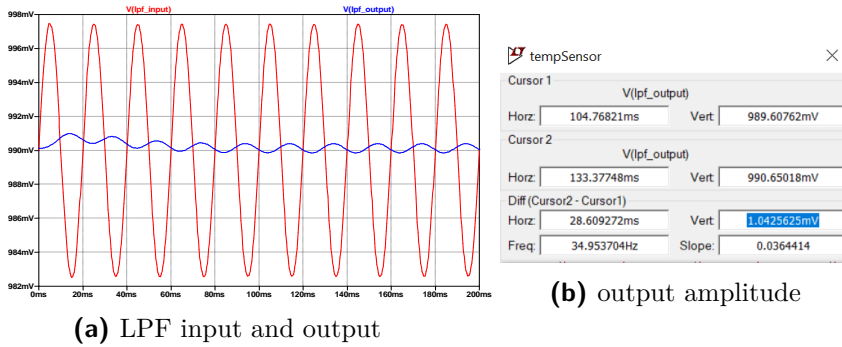


Figure 3.4: Low-pass filter noise suppression simulation results

As illustrated in figure 3.4 above, a 15 mV amplitude noise signal (corresponding to 1°C) is attenuated to 1 mVpp. After amplification, with a gain of 40, the noise will thus be only 40 mVpp or 20 mVp, meeting the "bellow 80 mVp requirement".

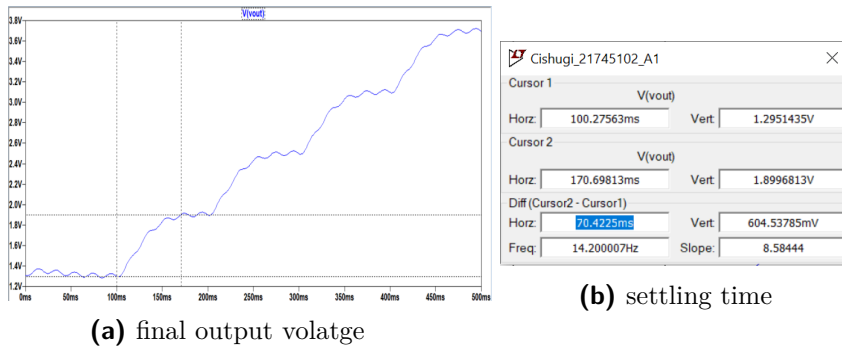


Figure 3.5: Low-pass filter rise time simulation results with the differential amplifier included

As illustrated in figure 3.5 above, the LPF rise time is 70.42 ms which is even better than the 83.91 ms designed for. The plot illustrates a 1°C step in temperature from 36°C

to 40°C(not full range, just for demonstration) and after each step, the rise time is 70.42 ms which meets the "bellow 100 ms settling time".

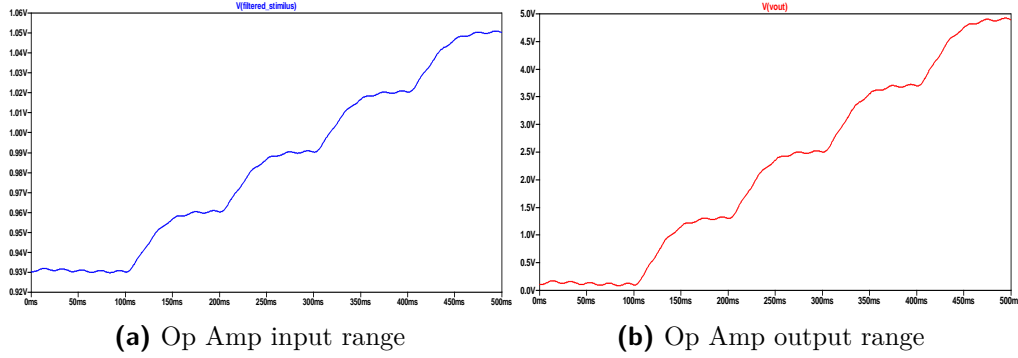


Figure 3.6: Full Op amp input and output range simulation results

Table 3.1 bellow records the measured full input and output ranges as well as the measured output voltages corresponding to temperatures between 34°C and 42°C.

T °C	34	35	36	37	38	39	40	41	42	Full range
Stimulus (mV)	930	945	960	975	990	1005	1020	1035	1050	120 mV
Vout (V)	0.1	0.7	1.3	1.9	2.5	3.1	3.7	4.3	4.9	4.8V

Table 3.1: measured full Op Amp input and output ranges

Hence, as designed for, VIN_max is 1050 mV and VIN_min is 930 mV.

Figure 3.7 bellow illustrates the total average current used by the temperature sensor circuit.

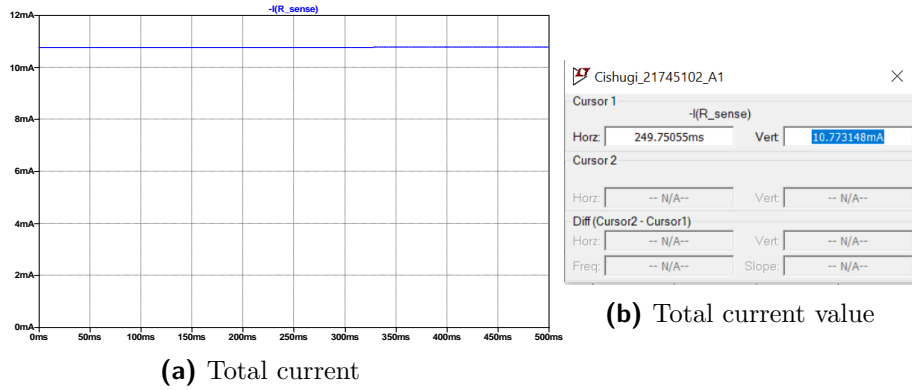


Figure 3.7: Total average current of temperature sensor circuit

Hence, the total average current used by the circuit is 10.77 mA, which is smaller than the 25 mA required threshold.

3.4. Summary

The Low pass filter successfully suppressed the noise and the differential amplifier produced a 4.8V range as designed for while the total current consumption stayed bellow 11mA.

Chapter 4

System and conclusion

4.1. System

Overall, the full circuit works as designed considering the simulation results in the previous section. The linear regulator outputs a 5VDC with very little to no noise and supplies it to the active low pass filter and the differential amplifier circuit. These together form a temperature sensor, the first building block of the health monitor system. This part alone of the system draws an average of 10.77mA from the 9V supply, leaving $(100\text{mA} - 10.77\text{mA}) = 89.23\text{mA}$ for the rest of the system. Using table 4.1 below, the calibration constant for the temperature sensor can be derived:

T °C	34	35	36	37	38	39	40	41	42
Stimulus (mV)	930	945	960	975	990	1005	1020	1035	1050
Vout (V)	0.1	0.7	1.3	1.9	2.5	3.1	3.7	4.3	4.9

Table 4.1: Temperatures and corresponding output voltage

$$\therefore T \text{ }^{\circ}\text{C} = \frac{5}{3} \cdot V_{\text{out}} + \frac{203}{6}$$

After calibration, the temperature value will be rounded to the nearest integer using quantisation.

4.2. Lessons learnt

- The theory behind a switchingmode regulator as well as design procedures to include it in a certain application.
- How to select a certain filter configuration and design it given a bandwidth and rise time specifications.
- The full design of a differential amplifier with a virtual ground given specific requirements.

Bibliography

- [1] Renesas Electronics Corporation, “Linear vs. switching regulators,” 2021. [Online]. Available: <https://www.renesas.com/cn/en/products/power-management/linear-vs-switching-regulators.html>
- [2] *LM78XX, LM78XXA 3-Terminal 1 A Positive Voltage Regulator*, LM7805 datasheet, Fairchild, September 2014.
- [3] *LM2595 SIMPLE SWITCHER® Power Converter 150-kHz 1-A Step-Down Voltage Regulator*, LM2595 datasheet, Texas Instruments, May 2016.
- [4] *TLC227x, TLC227xA: Advanced LinCMOS Rail-to-Rail Operational Amplifiers*, TLC2272 datasheet, Texas Instruments, March 2016.

Appendix A

Social contract

Sign and include.



UNIVERSITEIT•STELLENBOSCH•UNIVERSITY
jou kennisvenoot • your knowledge partner

E-design 344 Social Contract

2020

The purpose of this document is to establish commitment between the student and the organisers of E344. Beyond the commitment made here, it is not binding.

In the months preceeding the term, the lecturer (Thinus Booysen) and the Teaching Assistant (Michael Ritchie) spent countless hours to prepare for E344 to ensure that you get your money's worth and that you are enabled to learn from the module and demonstrate and be assessed on your skills. We commit to prepare for the module, to set the tests and assessments fairly, to be reasonably available, and to provide feedback and support as best and fast we can. We will work hard to give you the best opportunity to learn from and pass analogue electronic design E344.

Signature:  Date: 13 July 2020

I, **Elijah Seth Cishugi** have registered for E344 of my own volition with the intention to learn of and be assessed on the principals of analogue electronic design. Despite the potential publication of supplementary videos on specific topics, I acknowledge that I am expected to attend the lectures and lab sessions to make the most of these appointments and learning opportunities. Moreover, I realise I am expected to spend the additional requisite number of hours on E344 as specified in the yearbook.


I acknowledge that E344 is an important part of my journey to becoming a professional engineer, and that my conduct should be reflective thereof. This includes doing and submitting my own work, working hard, starting on time, and assimilating as much information as possible. It also includes showing respect towards the University's equipment, staff, and their time.

Signature:  Date: 16th / August / 2020

Appendix B

GitHub Activity Heatmap

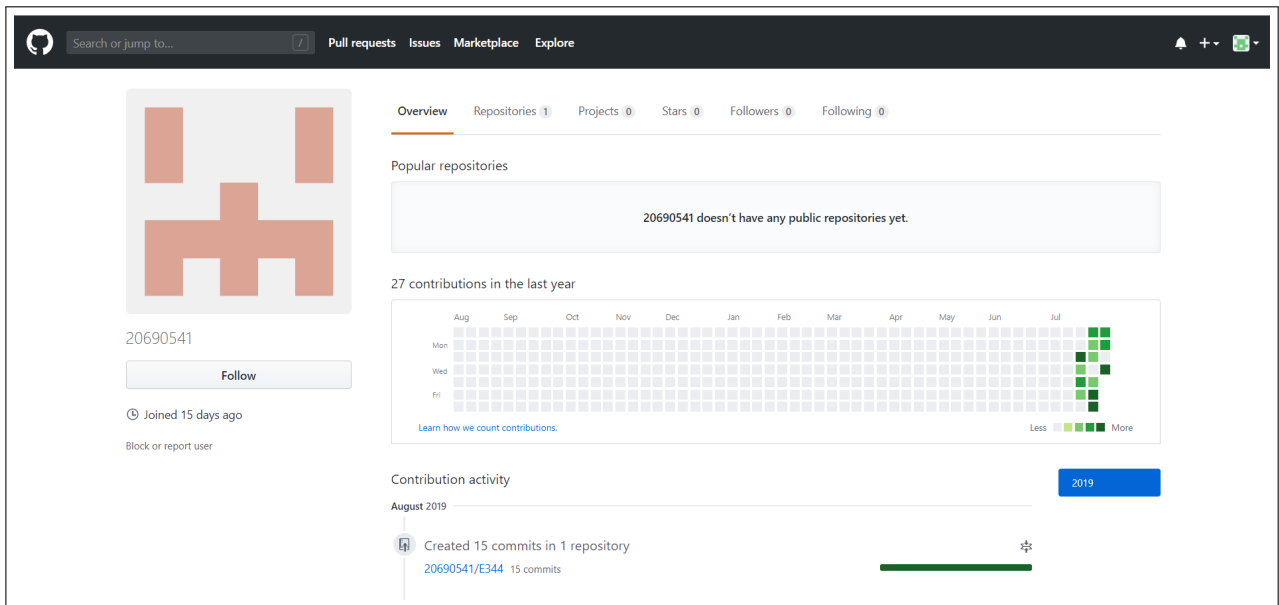Take a screenshot of your github version control activity heatmap and insert here.



Appendix C

Stuff you want to include

Lorem ipsum dolor sit amet, consectetur adipiscing elit. Ut purus elit, vestibulum ut, placerat ac, adipiscing vitae, felis. Curabitur dictum gravida mauris. Nam arcu libero, nonummy eget, consectetur id, vulputate a, magna. Donec vehicula augue eu neque. Pellentesque habitant morbi tristique senectus et netus et malesuada fames ac turpis egestas. Mauris ut leo. Cras viverra metus rhoncus sem. Nulla et lectus vestibulum urna fringilla ultrices. Phasellus eu tellus sit amet tortor gravida placerat. Integer sapien est, iaculis in, pretium quis, viverra ac, nunc. Praesent eget sem vel leo ultrices bibendum. Aenean faucibus. Morbi dolor nulla, malesuada eu, pulvinar at, mollis ac, nulla. Curabitur auctor semper nulla. Donec varius orci eget risus. Duis nibh mi, congue eu, accumsan eleifend, sagittis quis, diam. Duis eget orci sit amet orci dignissim rutrum.

Nam dui ligula, fringilla a, euismod sodales, sollicitudin vel, wisi. Morbi auctor lorem non justo. Nam lacus libero, pretium at, lobortis vitae, ultricies et, tellus. Donec aliquet, tortor sed accumsan bibendum, erat ligula aliquet magna, vitae ornare odio metus a mi. Morbi ac orci et nisl hendrerit mollis. Suspendisse ut massa. Cras nec ante. Pellentesque a nulla. Cum sociis natoque penatibus et magnis dis parturient montes, nascetur ridiculus mus. Aliquam tincidunt urna. Nulla ullamcorper vestibulum turpis. Pellentesque cursus luctus mauris.

Nulla malesuada porttitor diam. Donec felis erat, congue non, volutpat at, tincidunt tristique, libero. Vivamus viverra fermentum felis. Donec nonummy pellentesque ante. Phasellus adipiscing semper elit. Proin fermentum massa ac quam. Sed diam turpis, molestie vitae, placerat a, molestie nec, leo. Maecenas lacinia. Nam ipsum ligula, eleifend at, accumsan nec, suscipit a, ipsum. Morbi blandit ligula feugiat magna. Nunc eleifend consequat lorem. Sed lacinia nulla vitae enim. Pellentesque tincidunt purus vel magna. Integer non enim. Praesent euismod nunc eu purus. Donec bibendum quam in tellus. Nullam cursus pulvinar lectus. Donec et mi. Nam vulputate metus eu enim. Vestibulum pellentesque felis eu massa.

Quisque ullamcorper placerat ipsum. Cras nibh. Morbi vel justo vitae lacus tincidunt ultrices. Lorem ipsum dolor sit amet, consectetur adipiscing elit. In hac habitasse platea dictumst. Integer tempus convallis augue. Etiam facilisis. Nunc elementum fermentum wisi. Aenean placerat. Ut imperdiet, enim sed gravida sollicitudin, felis odio placerat quam, ac pulvinar elit purus eget enim. Nunc vitae tortor. Proin tempus nibh sit amet nisl. Vivamus quis tortor vitae risus porta vehicula.

Fusce mauris. Vestibulum luctus nibh at lectus. Sed bibendum, nulla a faucibus semper, leo velit ultricies tellus, ac venenatis arcu wisi vel nisl. Vestibulum diam. Aliquam pellentesque, augue quis sagittis posuere, turpis lacus congue quam, in hendrerit risus eros eget felis.

Maecenas eget erat in sapien mattis porttitor. Vestibulum porttitor. Nulla facilisi. Sed a turpis eu lacus commodo facilisis. Morbi fringilla, wisi in dignissim interdum, justo lectus sagittis dui, et vehicula libero dui cursus dui. Mauris tempor ligula sed lacus. Duis cursus enim ut augue. Cras ac magna. Cras nulla. Nulla egestas. Curabitur a leo. Quisque egestas wisi eget nunc. Nam feugiat lacus vel est. Curabitur consectetur.

Suspendisse vel felis. Ut lorem lorem, interdum eu, tincidunt sit amet, laoreet vitae, arcu. Aenean faucibus pede eu ante. Praesent enim elit, rutrum at, molestie non, nonummy vel, nisl. Ut lectus eros, malesuada sit amet, fermentum eu, sodales cursus, magna. Donec eu purus. Quisque vehicula, urna sed ultricies auctor, pede lorem egestas dui, et convallis elit erat sed nulla. Donec luctus. Curabitur et nunc. Aliquam dolor odio, commodo pretium, ultricies non, pharetra in, velit. Integer arcu est, nonummy in, fermentum faucibus, egestas vel, odio.

Sed commodo posuere pede. Mauris ut est. Ut quis purus. Sed ac odio. Sed vehicula hendrerit sem. Duis non odio. Morbi ut dui. Sed accumsan risus eget odio. In hac habitasse platea dictumst. Pellentesque non elit. Fusce sed justo eu urna porta tincidunt. Mauris felis odio, sollicitudin sed, volutpat a, ornare ac, erat. Morbi quis dolor. Donec pellentesque, erat ac sagittis semper, nunc dui lobortis purus, quis congue purus metus ultricies tellus. Proin et quam. Class aptent taciti sociosqu ad litora torquent per conubia nostra, per inceptos hymenaeos. Praesent sapien turpis, fermentum vel, eleifend faucibus, vehicula eu, lacus.